

Deputy Executive Information Engineers in A.P. Information Service-  
**NOTIFICATION NO: 29/2018 (GENERAL RECRUITMENT)**  
**INITIAL KEY**

1. An open circuited coil has \_\_\_\_\_.

**Infinite resistance and zero inductance**

2. An RC network has a capacitor  $C = 2\mu\text{F}$  in series with a resistor  $R = 1\text{M}\Omega$ . The time of 6 seconds will be equal to \_\_\_\_\_.

**three time constants**

3. In a RLC series resonant circuit at the half power points \_\_\_\_\_.

**The resistance equal to the resultant reactance**

4. A two port network is reciprocal if and only if

**$BC - AD = -1$**

5. A step function voltage is applied to a RLC series circuit having  $R = 1\Omega$ ,  $L = 1\text{H}$ , and  $C = 1\text{F}$ . The transient current response of the circuit would be \_\_\_\_\_.

**under damped**

6. A two terminal black box contains an element which can be R, L, C and M. As soon as the black box is connected to a DC voltage source, a finite non zero current is observed to flow through the element. The element is \_\_\_\_\_.

**a resistor**

7. The transfer function of an electrical lowpass RC network is \_\_\_\_\_.

$$\frac{1}{1 + RCs}$$

8. The DC gain of a system represented by the transfer function  $\frac{5}{(s + 2)(s + 3)}$  is \_\_\_\_\_.

9. A capacitor of 0.1F has a leakage resistance of 100kΩ across its terminals. Its quality factor at 10 rad/sec is \_\_\_\_\_.

$$10^5$$

10. The system is represented by the difference equation  $\ddot{y} + 5\dot{y} + 6y = u$ . The state vector matrices A, B, C, D are

$$A = \begin{bmatrix} 0 & 1 \\ -6 & -5 \end{bmatrix}, B = \begin{bmatrix} 0 \\ 1 \end{bmatrix}, C = [1 \quad 0], D = [0]$$

11. The output of the integral function  $\int_{-1}^1 (3t^2 + 1)\delta(t)dt$  is

$$1$$

12. A system has the input – output relation given by  $y(t) = T[x(t)] = x^2(t)$ , The system is \_\_\_\_\_.

**Non-linear, Time invariant**

13. The impulse responses of the systems are given by  $h_1(t) = e^{-2t}u(t)$  and  $h_2(t) = 2e^{-t}u(t)$ . These two systems  $h_1(t)$  and  $h_2(t)$  are connected in cascade. The impulse response of the overall system is \_\_\_\_\_.

$$2(e^{-t} - e^{-2t})u(t)$$

14. The Z-Transform of  $x[n] = -a^n u[-n-1]$  is \_\_\_\_\_.

$$\frac{z}{z - a}$$

15. The inverse Z transform of  $X(z) = \log\left(\frac{1}{1 - a^{-1}z}\right), |z| < a$ , \_\_\_\_\_.

$$-\frac{1}{n} a^n u[-n-1]$$

16. Fourier series coefficient of the  
signal  $(t) = \cos 4\pi t + \sin 6\pi t$

is \_\_\_\_\_.

$$a_{\pm 3} = \pm \frac{1}{2j}, a_{\pm 2} = \pm \frac{1}{2}$$

17. The DFT of  $x^*[n]$  is \_\_\_\_\_.

$$X^*[-k]_{\text{mod } N}$$

18. Consider a discrete time LTI system described by  $y[n] - \frac{1}{2}y[n-1] = x[n] + \frac{1}{2}x[n-1]$ . The frequency response  $H(e^{j\omega})$  of the system is \_\_\_\_\_.

$$\frac{1 + \frac{1}{2}e^{-j\omega}}{1 - \frac{1}{2}e^{-j\omega}}$$

19. If the Nyquist rate for  $x_a(t)$  is  $\Omega_s$ . The Nyquist rate for  $\frac{dt}{dt}$  is \_\_\_\_\_.

$$\Omega_s$$

20. How many complex multiplications are necessary in a radix 3 decimation in frequency FFT computation?

$$2N \log_3 N$$

21. A Si sample is doped with  $10^{17}$  As atoms/cm<sup>3</sup>. The equilibrium hole concentration at 300K is \_\_\_\_\_ ( $n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$ )

$$2.25 \times 10^3 \text{ cm}^{-3}$$

22. Consider two Si PN junction diodes, one long and one short (contacts within a diffusion length of the depletion region) but otherwise identical. Under identical forward bias voltage, which diode would have greater current flow?

**Short**

23. The \_\_\_\_\_ is (desirably) high for voltage controlled field effect transistors and low for current controlled bipolar junction transistors.

**Input Impedance**

24. While increasing the device temperature, the subthreshold source to drain leakage current of MOSFET will be \_\_\_\_\_.

**Increased**

25. The resistivity of the P region and N region of a Germanium diode are  $6\Omega\text{-cm}$  and  $4\Omega\text{-cm}$  respectively. The contact potential and the potential energy barrier are \_\_\_\_\_ and \_\_\_\_\_. (The given details are  $q = 1.6 \times 10^{-19}\text{C}$ ,  $n_i = 2.5 \times 10^{13}/\text{cm}^3$ ,  $\mu_p = 1800 \text{ cm}^2/\text{V-s}$ ,  $\mu_n = 3800 \text{ cm}^2/\text{V-s}$ , and  $V_T = 0.026\text{V}$  at  $300^\circ\text{K}$ ).

**0.1545V, 0.1545eV**


26. If a bipolar junction transistor has  $\beta = 100$  and the collector current is  $40\text{mA}$ . The emitter current is \_\_\_\_\_.

**40.4mA**

27. The reverse leakage current of the transistor when connected in common base (CB) configuration is  $0.2\mu\text{A}$  and it is  $20\mu\text{A}$  when the same transistor is connected in common emitter (CE) configuration. The large signal dc current gain of the transistor in CE configuration is \_\_\_\_\_. (Assume  $I_B = 30\text{mA}$ )

**99**

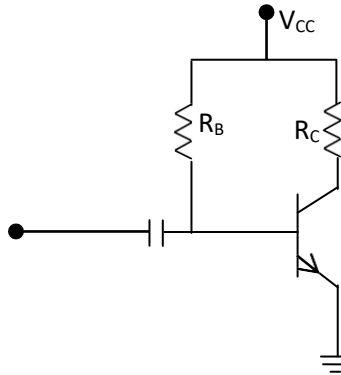28. What is the value of  $R_B$  and  $R_C$  in the circuit given below? The data as follows:  $I_{CQ} = 1\text{mA}$ ,  $V_{CEQ} = 16\text{V}$ ,  $V_{CC} = 10\text{V}$ ,  $V_{BE(ON)} = 0.7\text{V}$  and  $\beta = 100$ .



**0.93M $\Omega$ , 4k $\Omega$**

29. The stability factor is defined as

**a. The rate of change of the  $I_C$  with respect to  $I_{C0}$ , keeping  $I_B$  and  $\beta$  constant**

30. An N channel JFET has  $I_{DSS} = 8\text{mA}$ , and  $V_P = -5\text{V}$ . The  $V_{DS(\text{min})}$  and  $I_{DS}$  are \_\_\_\_\_ and \_\_\_\_\_ for  $V_{GS} = -2\text{V}$  in the pinch off region.

**3V, 2.88mA**

31. For reverse biased PN junction, the current through the junction increases abruptly at \_\_\_\_\_

**Breakdown voltage**

32. The LED light is emitted because

**recombination of charge carriers take place**

33. Find the correct match between Group A and Group B

Group A

Group B

(i) Varactor diode

(a) Voltage reference

(ii) PIN diode

(b) High frequency switch

- (iii) Zener diode                      (c) Tuned circuit  
 (iv) Schottky diode                    (d) current controlled attenuator

**(i) – c, (ii) – d, (iii) – a, (iv) – b**

34. Match items in Group A with items Group B, most suitably

Group A	Group B
(i) LED	(a) Heavily doping
(ii) Avalanche diode	(b) coherent radiation
(iii) Tunnel diode	(c) spontaneous emission
(iv) LASER	(d) current gain

**(i) – c, (ii) – d, (iii) – a, (iv) – b**

35. The process is to arrange the atom in single crystal fashion upon a single crystal substrate is \_\_\_\_\_.

**Epitaxial growth**

36. Films with thickness greater than  $100\mu\text{m}$  are usually made by \_\_\_\_\_ technology.

**Thick**

37. Buried layer is a heavily doped  $n^+$  layer sandwiched between the P type substrate and N type epitaxial collector to \_\_\_\_\_ the collector series resistance of the IC transistor.

**reduce**

38. Arrange the basic processes in order to use in the silicon planar technology.

**Substrate preparation, epitaxial growth,  $\text{SiO}_2$  growth, photolithography, diffusion, metallization**

39. The film technology provides greater precision in manufacturer is \_\_\_\_\_.

**thin**

40. Voltage divider bias \_\_\_\_\_.

**Can be essentially independent of  $\beta_{DC}$**

41. Ideally, a dc load line is a straight line drawn on the collector characteristic curves between

**the  $V_{CE}(\text{cut off})$ , and  $I_C(\text{sat})$**



42. A MOSFET differs from a JFET mainly because  
**the JFET has a PN junction**

43. A certain D-MOSFET is biased at  $V_{GS} = 0V$ . Its data sheet specifies  $I_{DSS} = 20mA$  and  $V_{GS(off)} = -5V$ . the value of the drain current is \_\_\_\_\_.

**20mA**


44. In a certain FET circuit,  $V_{GS} = 0V$ ,  $V_{DD} = 15V$ ,  $I_{DSS} = 15mA$ , and  $R_D = 470\Omega$ . If  $R_D$  is decreased  $330\Omega$ ,  $I_{DSS}$  is \_\_\_\_\_.

**15mA**

45. A class C amplifier is driven by a 200kHz signal. The transistor is on for  $1\mu s$  and the amplifier is operating over 100% of its load line. If  $I_{C(sat)} = 100mA$  and  $V_{CE(sat)} = 0.2V$ . The average power dissipation is \_\_\_\_\_.

**4mW**

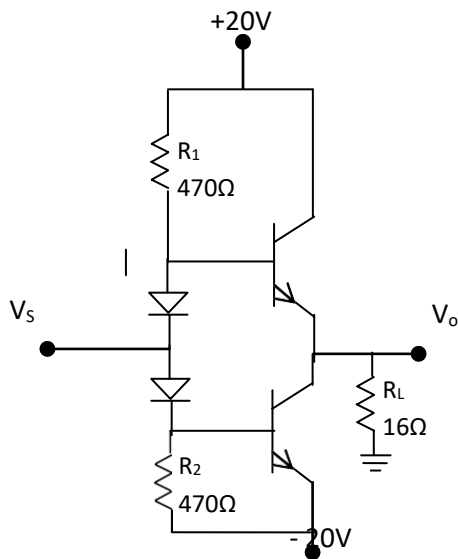46. The ideal maximum peak output voltage and current for the circuit shown below is \_\_\_\_\_ and \_\_\_\_\_.



**20V, 1.25A**

47. A class A power amplifier delivers 5W to a load with an input signal power of 100mW. The power gain is \_\_\_\_\_.

**50**

48. Both stages in a certain 2 stage amplifier have a lower critical frequency of 500Hz and an upper critical frequency of 80kHz. The overall bandwidth is \_\_\_\_\_.

**50.7kHz**

49. A series regulator has an output voltage of 9V. If the opamp's closed loop gain is 3, what is the value of the reference voltage?

**3V**

50. A regulator has a no load output voltage of 10V and a full load output voltage of 9.9v. The percent of load regulation is \_\_\_\_\_.

**1.01**

51. An inverting amplifier has a closed loop gain of 25. The opamp has an open loop gain of  $10^5$ . If another opamp with an open loop gain of  $2 \times 10^5$  is substituted in the configuration, the closed loop gain \_\_\_\_\_.

**remains at 25**

52. Which statement is wrong for ideal characteristics of opamp \_\_\_\_\_.

**Slew rate is zero**

53. What is the breakdown voltage of the precision diode made up of silicon material?

**0.7V/A<sub>OL</sub>**

54. The Notch filter is a \_\_\_\_\_.

**filter to eliminate a single frequency in the input signal**

55. How many opamp based voltage comparators are used in 555 timer IC?

**2**

56. In 555 timer astable mode operation, the fundamental frequency of the output waveform is \_\_\_\_\_.

**(1)  $T = 0.693(R_A + 2R_B)C$**

57. A lowpass Butterworth filter to band pass Butterworth filter transformation function will be \_\_\_\_\_.

$$s \rightarrow \frac{s^2 + \omega_0^2}{(\omega_h - \omega_l)s}$$

58. An amplifier has a power gain of 23dB. If the input is 1mW, what is the output?

**199.5mW**

59. The advantage of linear regulator is

**accuracy of control**

60. The switching regulator has \_\_\_\_\_ efficiency

**high**

61. Which statement is wrong for the general rules that should be considered when using heat sinks?

**Give excessive torque on the mounting hardware**


62. How might square wave be generated from a triangular source?

**Pass the output of the triangular wave generator into a comparator**

63. Binary equivalent of gray code number 10110101 is \_\_\_\_\_.

**11011001**

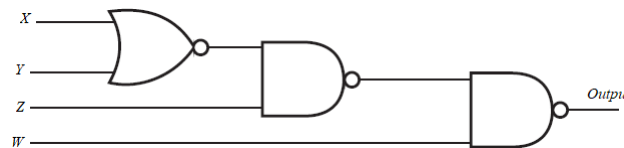64. The Boolean expression of the figure shown below is \_\_\_\_\_.



$$\overline{X}Y.Z + \overline{W}$$

65. The Consensus theorem says that \_\_\_\_\_.

$$XY + \overline{X}Z + YZ = XY + \overline{X}Z$$

66. Given that IC7483 is a 4 bit parallel adder chip, how do you build a 16 bit parallel adder circuit?

**by a cascaded arrangement of 4 IC7483s**

67. Identify the incorrect statement

**D flip flop is same as  
D latch**

68. An 8 bit binary ripple up counter with a modulus of 256 is holding the count 01111111.what will be the count after 135 clock pulses?

**00000110**

69. A binary ripple counter is capable of counting the number of items passing on a conveyer belt. Each time an item passes a given point, a pulse is generated that can be used to as a clock input. If the maximum number of items to be counted is 8000,\_\_\_\_\_number of flip flops required.

**13**

70. A 4 bit ring counter is in turn clocked by a 10MHz clock signal. The frequency and duty cycle of the output flip flop are\_\_\_\_\_and\_\_\_\_\_.

**2.5MHz, 25%**

71. A 100 stage serial in serial out shift register is clocked at 100kHz. How long will be the data be delayed in passing through this register?

**1ms**

72. Minterm and Maxterm Boolean functions of  $f(A, B, C) = \prod(0,3,7)$  is \_\_\_\_\_,

$$A\bar{B} + \bar{B}C + B\bar{C}, (A+B+C)(\bar{B} + \bar{C})$$

73. A dynamic RAM consists of \_\_\_\_\_

**1 transistor and 1 capacitor**

74. The access time of ROM using bipolar transistor is about \_\_\_\_\_.

**1μsec**

75. Which is known as flash converter \_\_\_\_\_.

**parallel ADC**

76. A 10 bit DAC given a maximum output of 10.23V. The resolution is

**(1) 10mV**

77. An 8 bit successive approximation ADC has full scale reading of 2.55V and its conversion time for an analog input of 1V is 20μs. the conversion time for a 2V input will be

**20μs**

78. A 6 bit ladder DAC has input 101001. For 1=10V and 0 = 0V, the output is

**6.51**

79. In an 8085 microprocessor, the shift registers which store the result of an addition and the overflow bit are respectively.

**A and F**

80. In an 8085 microprocessor, which one of the following instructions changes the content of the accumulator?

**SBI BEH**

81. A transfer function has two zeros at infinity. Then the relation between the numerator degree (M) and the denominator degree (N) of the transfer function is

**(M = N-2)**

82. The differential equation of the SISO system is given by 
$$\frac{d^2 y}{dt^2} + \frac{1}{dt} dy + 10y = 5 \frac{du}{dt} - 3u,$$
 where  $y$  denotes output and  $u$  represents input. For an input  $u(t)$  with zero initial conditions the above system produces the same output as with no input and with initial conditions  $y'(0-) = -4, y(0-) = 1$ . Input  $u(t)$

$$\frac{1}{5}\delta(t) - \frac{7}{25}e^{\frac{3}{5}t}u(t)$$




83. A control system is defined by the following differential equation

$$\frac{d^2x}{dt^2} + 6\frac{dx}{dt} + 10x = 12(1 - e^{-2t})$$

. The response of the system as  $t \rightarrow \infty$  is

**x=2.4**

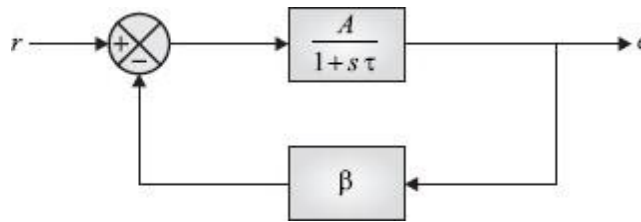84. In the feedback system shown in figure below, the time constant of the closed loop system will be




$$\frac{\tau}{1 + A\beta}$$

85. Despite the presence of negative feedback control system still have problems of instability because the


**components used have non-linearity**

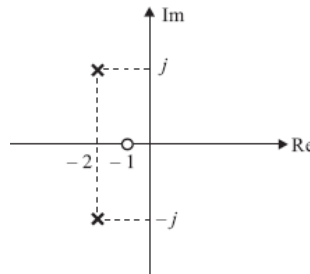86. The pole zero plot of open loop transfer function system shown below and the steady state gain is 2, the transfer function of the system will be given by



$$\frac{10(s + 1)}{s^2 + 4s + 5}$$

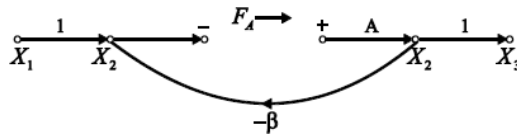87. Consider the following single loop feedback structure illustrating the return difference



The return difference of A is

$$1 + A\beta$$

88. Consider the following statements regarding advantages of closed loop negative feedback control systems over open loop systems.

- The overall reliability of the closed loop system is more than that of open loop system
- The transient response in a closed loop system decays more quickly than open loop system
- In an open loop system, closing of the loop increases the overall gain of the system
- In the closed loop system, the effect of variation of component parameters on its performance is reduced.

**(i) and (ii)**

89. A forcing function  $(t^2 - 2t)u(t-1)$  is applied to a linear system. The Laplace transform of the forcing function is

$$\frac{2 - s^2}{s^3} e^{-s}$$

90. Compensator which adds negative phase to system over specified frequency range is called

**Lag**

91. In control systems, when maximum value is subtracted from step value and result is divided by step value, result is called as

**Percentage undershoot**

92. Lead compensator has a pole to the

**left of zero**

93. A first order dynamic system is represented by the differential equation  $5\dot{x}(t) + x(t) = u(t)$ . The corresponding transfer function and state space representation are

$$H(s) = \frac{1}{1 + 5s} \quad \text{and} \quad \dot{\mathbf{x}} = -\mathbf{0.2x} + \mathbf{0.5u}, \mathbf{y} = \mathbf{0.4x}$$

94. Consider the system represented by  $\dot{x} = Ax + Bu$ , where  $A = \begin{bmatrix} 0 & 5 \\ 0 & 0 \end{bmatrix}$  and  $B = \begin{bmatrix} 1 \\ 0 \end{bmatrix}$ . The associated state transition matrix is

$$\Phi(t,0) = \begin{bmatrix} 1 & 5t \\ 0 & 1 \end{bmatrix}$$

95. A system has a characteristic equation stable  $s^3 + Ks^2 + (1+K)s + 6 = 0$ . The range of K for a system is \_\_\_\_\_.

**K>2**

96. Use of Routh array to assist in computing the roots of the polynomial function,  
 $P(s) = 2s^3 + 2s^2 + s + 1 = 0$ .

$$S_1 = -1, S_{2,3} = \pm j \frac{1}{\sqrt{2}}$$

97. A system has a characteristic equation  $s^3 + 10s^2 + 2s + 30 = 0$ . The system is\_\_\_\_\_.

**unstable**

98. The amplitude of the closed loop response is reduced approximately to one fourth of the maximum value in one oscillatory period. This definition belongs to

**Asymptote**

99. A method of selecting one or two parameters using the root locus method is called as\_\_\_\_\_.

**Angle of departure**

100. All zeros of a transfer function lies in the left hand side of the S –plane, then the system is\_\_.

**Minimum phase**

101. The relationship between autocorrelation function(ACF) and power spectral density (PSD) is

**Fourier transform of ACF is equal to PSD**

102. For a particular case of amplitude modulation (AM) using sinusoidal modulating wave, the percentage modulation is 20%. The average power in the carrier signal is\_\_\_\_\_.

**98%**

103. In AM, spectral overlap is said to occur if the lower sideband for positive frequencies overlaps with its image for negative frequencies. What condition must the modulated wave satisfy if you are to avoid spectral overlap? Hint: the message signal bandwidth is  $W$ .

Carrier frequency  $f_c > W$

104. Which statement is correct for envelope detector

**The carrier frequency is large compared to the message bandwidth**

105. To minimize the granular noise, the step size must be \_\_\_\_\_.

**small**

106. In PCM for  $Q$  quantity levels, the number of pulses  $P$  in a code group is given by \_\_\_\_\_

**$\log_2(Q)$**

107. Pulse width modulation involves

**Varying width of pulses in the pulse train according to instantaneous variations of message signal**

108. Consider the signal  $x(t) = m(t) \cos 2\pi f_c t + \hat{m}(t) \cos 2\pi f_c t$  where  $\hat{m}(t)$  denotes the Hilbert transform of  $m(t)$  and the bandwidth of  $m(t)$  is very small compared to  $f_c$ . The signal  $x(t)$  is a \_\_\_\_\_.

**band pass signal**

109. The modulation scheme commonly used for transmission from GSM mobile terminal is \_\_\_\_\_.

**Gaussian Minimum Shift Keying**

110. A zero mean white noise is passed through an ideal low pass filter of bandwidth 10kHz. The output is the uniformly sampled with sampling period  $t_s = 0.03\text{m/sample}$ . The samples so obtained would be \_\_\_\_\_.

**statistically independent**

111. In what type of multiplexing does each signal occupy the entire bandwidth of the channel?

**TDM**

112. The ability of the receiver to select the wanted signals among the various incoming signals is termed as \_\_\_\_\_.

**Selectivity**

113. A 400W carrier is amplitude modulated with  $m = 0.75$ . The total power in AM is \_\_\_\_\_.

**512W**

114. Non-coherent detection is not possible for

**PSK**

115. A telephone exchange has 9000 subscribers. If the number of calls originating at peak time is 10000 in one hour, the calling rate is \_\_\_\_\_.

**1.11**

116. If  $C$  is the noise channel capacity bits/s,  $\mathcal{f}$  is bandwidth in Hz and  $S/N$  is signal to noise ratio, then

$$C = \mathcal{f} \log_2 \left( 1 + \frac{S}{N} \right)$$

117. Consider the following statements

- The amplitude of an FM wave is constant
- FM is more immune to noise than AM
- FM broadcasts operate in upper VHF and UHF frequency ranges
- FM transmitting and receiving equipment are simpler as compared to AM transmitting and receiving equipment.

Which of the above are correct?

**(i), (ii), (iii)**

118. When the channel is noisy. Producing a conditional probability of error  $\rho = 0.5$ ; the channel capacity and entropy function will be \_\_\_\_\_ and \_\_\_\_\_.

**0 and 1**

119. If transmission bandwidth is doubled in FM, SNR is\_\_\_\_\_.

**decreased four times**

120. The bandwidth of DSB suppressed carrier modulation system when the modulating frequency varies between 500Hz and 5kHz is

**9kHz**

121 A super heterodyne receiver is to operate in the frequency range 550kHz – 1650kHz, with the

intermediate frequency of 450kHz. Let  $R = \frac{C_{\min}}{C_{\max}}$  denote the required capacitance ratio of the local oscillator and  $I_f$  represents the image frequency in (kHz) of the incoming signal. If the receiver is tuned to 700kHz, then R and  $I_f$  will be\_\_\_\_\_.

$$R = 4.41, I_f = \mathbf{1600}$$

122. Given  $A = 2a_x + 4a_y - 3a_z$  and  $B = a_x - a_y$ . The  $A \times B$  is\_\_\_\_\_.

$$\mathbf{-3a_x - 3a_y - 6a_z}$$

123. Gauss's law states that\_\_\_\_\_.

**The total flux out of a closed surface is equal to the net charge within the surface**

124. Divergence of the vector field A at the point P is defined by\_\_\_\_\_.

$$\lim_{\Delta v \rightarrow 0} \frac{\oint A \cdot dS}{\Delta v}$$

125. Five equal point charges,  $Q = 20nC$  are located at  $x = 2,3,4,5,6m$ . The potential at the origin is\_\_\_\_\_.

**261V**

126. The intrinsic impedance for partially medium is\_\_\_\_\_.

$$\sqrt{\frac{j\omega\mu}{\sigma + j\omega\epsilon}}$$



127. The skin depth at a frequency of 1.6MHz in aluminum is \_\_\_\_\_, where  
 $\sigma = 38.2 \text{ MS/m}$ ,  $\mu_r = 1$ .

**64.4μm**

128. The voltage standing wave ratio (VSWR) is calculated by \_\_\_\_\_.

$$\frac{1 + |\Gamma_R|}{1 - |\Gamma_R|}$$

129. The major difference between the rectangular and cylindrical waveguides as power transmitters when each operates in its dominant mode.

### Geometrical factor

130. A loss-less air dielectric cylindrical waveguide of inside diameter 3cm, is operated at 14GHz. For the  $\text{TM}_{11}$  mode propagating in the +Z direction, the wave impedance is \_\_\_\_\_.

**185Ω**

131. An air filled rectangular wave guide has dimensions  $a = 2 \text{ cm}$ ,  $b = 1 \text{ cm}$ . The range of frequencies over which the guide will operate single mode ( $\text{TE}_{10}$ ) \_\_\_\_\_.

**7.5 – 15 GHz**

132. A  $50\Omega$  lossless transmission line is terminated by a load impedance,  $Z_L = 50 - j75\Omega$ . If the incident power is 100mW, the power dissipated by the load is \_\_\_\_\_.

**64 mW**

133. The directivity of an antenna is the \_\_\_\_\_ value of its directive gain.

**maximum**

134. A conductor of a length \_\_\_\_\_ normal to an infinite conducting plane forms a monopole antenna.

**L/2**

135. A Hertzian dipole of length  $L=2\text{m}$  operates at 1MHz. If the copper conductor has

$\sigma_c = 57 \text{ MS/m}$ ,  $\mu_r = 1$ , and radius  $a = 1 \text{ mm}$ , then the radiation efficiency is \_\_\_\_\_.

**29.4%**

136. A 1cm radius circular loop antenna has N turns and operates at 100MHz. If radiation resistance is  $10\Omega$ , then N will be \_\_\_\_\_.

**515**

137. Identify the drawbacks of RADAR.

**It has very narrow coverage**

138. The RADAR acronym is\_\_\_\_\_.

**Radio detection and ranging**

139. Identify the wrong components in an optical transmitter

**photo detector**

140. The single mode fibers support only the\_\_\_\_\_mode.

**HE<sub>11</sub>**


141. In graded index fiber, the refractive index\_\_\_\_\_inside the core.

**decreases gradually**

142. Signal transmission in fiber optic communication systems takes place through the \_\_\_\_\_ modes only.

**Guided mode**

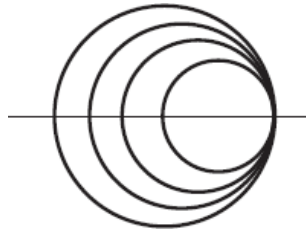143. Many circles are drawn in a Smith chart used for transmission line calculations. The circle shown in the figure represent\_\_\_\_\_.




**Constant resistance circles**

144. A transmission line is distortion less if\_\_\_\_\_.

**LG = RC**

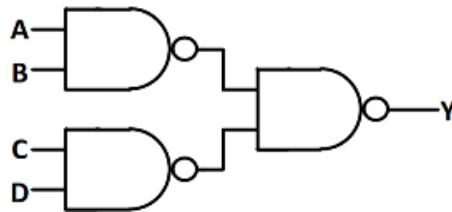145. In the logic circuit shown in the figure, Y is given by



**$Y = AB + CD$**

146. The transmitted signal in a GSM system is of 200 kHz bandwidth and 8 users share a common bandwidth using TDMA. If at a given time 12 users are talking in a cell, the total bandwidth of the signal received by the base station of the cell will be at least (in kHz)

---

**400 kHz**

147. An air-filled rectangular waveguide has inner dimensions of 3 cm X 2 cm. The wave impedance of the TE<sub>20</sub> mode of propagation in the waveguide at a frequency of 30 GHz is (free space impedance  $\eta_0 = 377 \Omega$ )

**400  $\Omega$**

148. A two-port network is known to have the following scattering matrix. If port 2 is terminated with a matched load, what is the return loss seen at port 1

$$[s] = \begin{bmatrix} 0.15 \angle 0^\circ & 0.85 \angle -45^\circ \\ 0.85 \angle 45^\circ & 0.2 \angle 0^\circ \end{bmatrix}$$

**16.5dB**

149. A magnetic field strength of 5  $\mu A/m$  is required at a point on  $\theta = \pi/2$ , 2 km from an antenna in air. Neglecting ohmic loss, how much power must the antenna transmit if it is a half-wave dipole?

**144 mW**

150. For a plastic fiber, refractive index of core is 1.6 and refractive index of cladding is 1.49, then numerical aperture is equal to

**0.58**